

Final Examination

Notice: Please turn off any types of handheld devices, and leave them far from reach. Use only standalone calculators for calculation if it is needed. The examination takes 100 minutes. 只需繳回答案紙，題目紙請同學保留。

- (11%) Derive a second-order differential equation that shows how the output $v_2(t)$ of the circuit shown in Fig. 1 is related to its input $v_s(t)$.
- (11%) Find $v_c(t)$ for $t > 0$ for the circuit shown in Fig. 2.

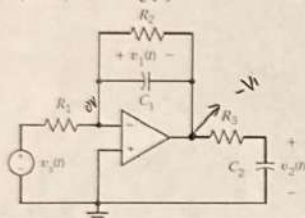


Fig. 1

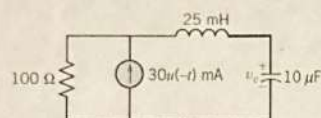


Fig. 2

- (11%) Find $i_L(t)$ when $t > 0$ for the circuit of Fig. 3. Assume a steady-state condition exists before $t = 0^-$.
- (11%) The circuit shown in Fig. 4 is at steady state before the switch closes. Determine the capacitor voltage $v(t)$, a complete response, for $t > 0$.

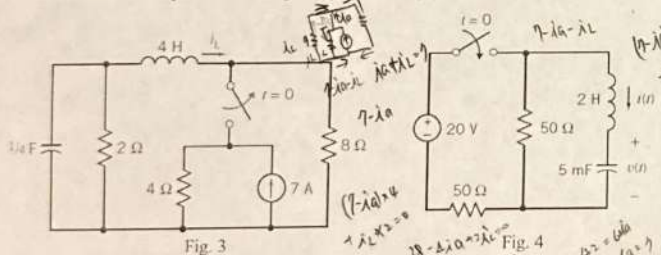


Fig. 3

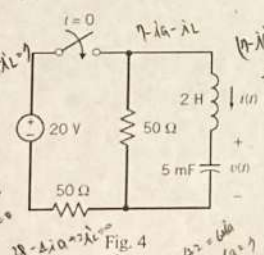


Fig. 4

- (10%) Determine the output voltage $v_a(t)$ for the circuit shown in Fig. 5.

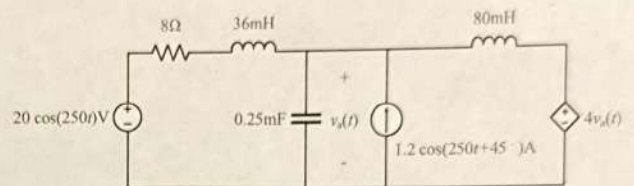


Fig. 5

- (11%) Determine the output voltage $v_o(t)$ when the circuit shown in Fig. 6 is at steady state and its input is $v_s(t) = 25 \cos(100t - 15^\circ)$ V.
- (11%) Find the Thevenin equivalent circuit for the circuit in Fig. 7.

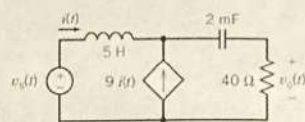


Fig. 6

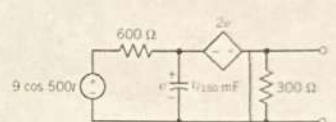


Fig. 7

- (11%) Determine the output voltage $v_o(t)$ of the circuit shown in Fig. 8 when its input is: $v_s(t) = 1.2 \cos(400t + 20^\circ)$ V.

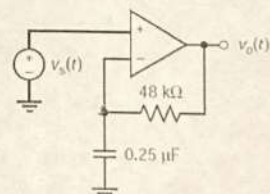


Fig. 8

- (13%) Determine the complete response of $i_o(t)$ in the circuit shown in Fig. 9. Assume the switch will open at $t = 0$. Your solution has to show both the cases: $t \leq 0$ and $t > 0$.

Move on to the next page

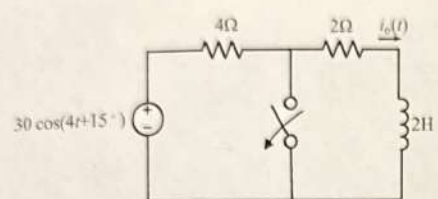


Fig.9