

Final-term Examination

Notice: Please turn off any types of handheld devices, and leave them far from reach. Use only standalone calculators for calculation if it is needed. The examination takes 100 minutes. 只需繳回答案紙，題目紙請同學保留。

1. (10%) Find Norton equivalence of the circuit shown in Fig. 1.

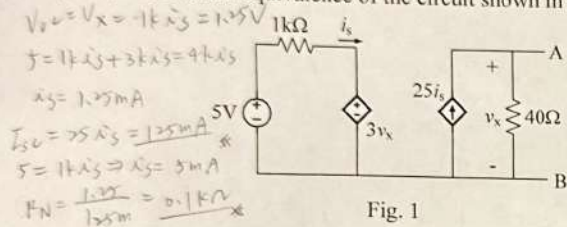


Fig. 1

2. (10%) Given that $0 \leq R \leq \infty$ in the circuit of Fig. 2, consider two observations:

- Observation 1: When $R = 8\Omega$ then $v_R = 15V$ and $i_R = 3A$.
- Observation 2: When $R = 8\Omega$ then $v_R = 16V$ and $i_R = 12A$.

Determine the maximum value of $p_R = i_R v_R$ and the value of R that causes p_R to be maximal.

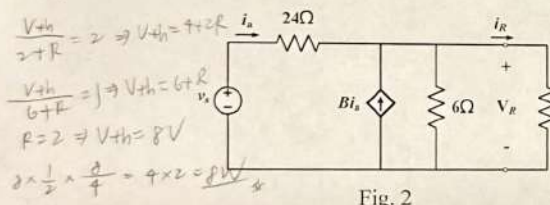


Fig. 2

3. (10%) Find the Thévenin equivalent circuit for the circuit shown in Fig. 3.

$$\left[\frac{R_1}{R_1+1} + \frac{R_2}{R_2+1} - \frac{R_3}{R_3+1} \right] V_{in} = \frac{V_{th}}{R_3}$$

$$\left[\frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1 R_2 R_3} - \frac{R_3}{R_3+1} \right] V_{in} = \frac{V_{th}}{R_3}$$

$$V_{th} = \frac{R_3 [R_1 R_2 + R_1 R_3 + R_2 R_3 - R_3 (R_3+1)]}{R_1 R_2 R_3 + R_1 R_3 + R_2 R_3 - R_3 (R_3+1)} V_{in}$$

$$V_{oc} = -V_A$$

$$\frac{6V}{8} + 0.75V_{oc} = \frac{V_{oc}}{4}$$

$$0.75V_{oc} = \frac{V_{oc}}{4} - \frac{6V}{8}$$

$$0.75V_{oc} = \frac{V_{oc}}{4} - \frac{3V}{4}$$

$$0.75V_{oc} + \frac{3V}{4} = \frac{V_{oc}}{4}$$

$$\frac{3V}{4} = \frac{V_{oc}}{4} - 0.75V_{oc}$$

$$\frac{3V}{4} = \frac{V_{oc} - 3V_{oc}}{4}$$

$$\frac{3V}{4} = \frac{-2V_{oc}}{4}$$

$$3V = -2V_{oc}$$

$$V_{oc} = -1.5V$$

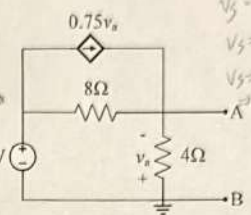


Fig. 3

$$V_{oc} = 4V$$

$$V_s = 8 \times 4 = 32V$$

$$V_s = 3 \times 8 = 24V$$

$$V_s = 12V$$

$$I_{sc} = 2A$$

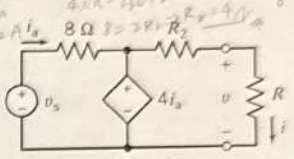


Fig. 4

4. For the circuit shown in Fig. 4, the open circuit voltage is $v_{oc} = 8V$, and short-circuit current is $i_{sc} = 2A$. Determine:
- (6%) The voltage source voltage v_s and the resistance R_2 .
 - (6%) The resistance R that maximizes the power delivered to the resistor to the right of the terminals, and the corresponding maximum power.

5. (14%) Figure 5 shows a voltage-controlled current source (VCCS) structured by an OP amplifier. Derive solutions of v_{out} and i_{out} in terms of v_{in} , R_1 , R_2 , R_3 , R_4 and R_L .

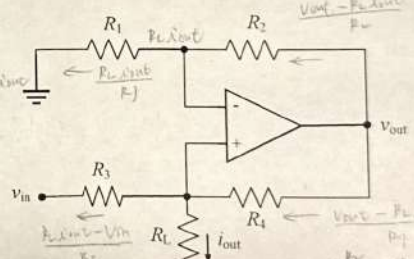


Fig. 5

6. (11%) Find v_o and i_o for the circuit of Fig. 6.

$$\left[\frac{R_1}{R_1+1} + \frac{R_2}{R_2+1} - \frac{R_3}{R_3+1} \right] V_{in} = \frac{V_{th}}{R_3}$$

$$\left[\frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1 R_2 R_3} - \frac{R_3}{R_3+1} \right] V_{in} = \frac{V_{th}}{R_3}$$

$$V_{th} = \frac{R_3 [R_1 R_2 + R_1 R_3 + R_2 R_3 - R_3 (R_3+1)]}{R_1 R_2 R_3 + R_1 R_3 + R_2 R_3 - R_3 (R_3+1)} V_{in}$$

$30i_0 + 20i_0 + \frac{v_0}{5k} = 0 \Rightarrow v_0 = -15V$
 $\frac{15}{3k} + \lambda_0 + \frac{-15}{4k} = 0 \Rightarrow \lambda_0 = 3mA + 3.75mA = 6.75mA$
 $0.5mA + \frac{3-v_0}{3k} = 0 \Rightarrow 0.5mA = \frac{v_0}{3k} \Rightarrow v_0 = 1.5V$
 $\frac{3-2}{3k} = \lambda_0 + \frac{12}{3k}$
 $-9 = 30\lambda_0 + 12$
 $\lambda_0 = \frac{-21}{30k} = -0.7mA$
 $\lambda_0 = \frac{-21}{30k}$

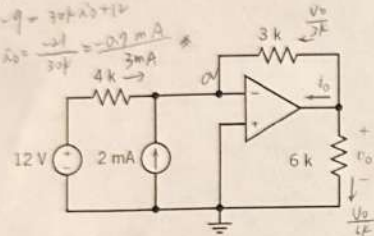


Fig. 6

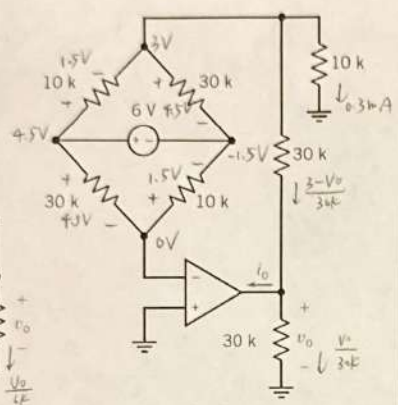


Fig. 7

7. (11%) Find v_o and i_o for the circuit shown in Fig. 7.
8. (11%) For the OP amplifier circuit in Fig. 8(a), calculate alternatively v_o with a finite gain model illustrated in Fig. 8(b) given $A = 10^5$, $R_o = 100\Omega$, and $R_i = 500k\Omega$. The circuit resistors are $R_s = 10k\Omega$, $R_f = 50k\Omega$, and $R_a = 25k\Omega$.

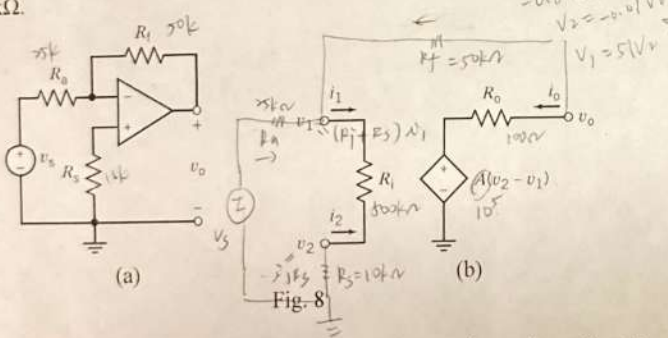


Fig. 8

9. (11%) In the circuit shown in Fig. 9(a), a voltage v_b is used to adjust the relationship between the input v_s and output v_o . Determine values of R_4 and

v_b that cause the circuit input and output to have the relationship specified by the graph shown in Fig. 9(b).

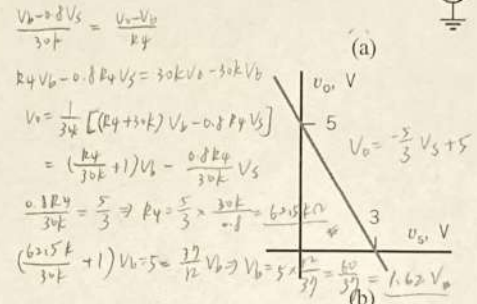
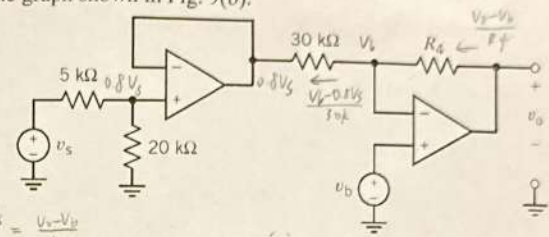


Fig. 9

$$\frac{V_s - \lambda_1(R_i + R_s)}{25k} + \frac{V_o - \lambda_1(R_i + R_s)}{50k} = \lambda_1$$

$$\frac{V_s - \lambda_1 \times 510k}{25k} + \frac{V_o - \lambda_1 \times 510k}{50k} = \lambda_1 \Rightarrow \frac{V_o}{50k} = (\frac{510k}{25k} + 1 + \frac{510k}{25k}) \lambda_1 - \frac{V_s}{25k}$$

$$\frac{V_o - \lambda_1 \times 510k}{50k} + \frac{V_o - 10^5 [\lambda_1 R_s - \lambda_1 (R_s + R_f)]}{50k} = 0$$

$$(\frac{1}{100} + \frac{1}{25k}) V_o = [\frac{510k}{50k} - 10^3 10k - 510k \times 10^3] \lambda_1$$

$$\frac{501}{50000} V_o = -510k \lambda_1$$

$$\lambda_1 = \frac{501}{5 \times 10^4 (-510k)} = -1.96 \times 10^{-11} V_s$$

$$\frac{V_o}{50k} = \frac{1 \times 10^3}{5} \times 1.96 \times 10^{-11} - \frac{V_s}{25k}$$