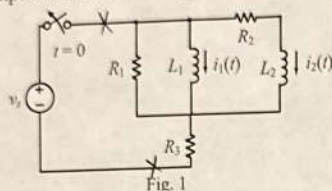



Midterm Examination

Notice: Please turn off any types of handheld devices, and leave them far from reach. Use only standalone calculators for calculation if it is needed. The examination takes 90 minutes. 只需繳回答案紙，題目紙請同學保留。

1. (11%) Represent the circuit shown in Fig. 1 by a differential equation for $t > 0$, when the input is v_s and the output is $i_2(t)$ of the inductor.



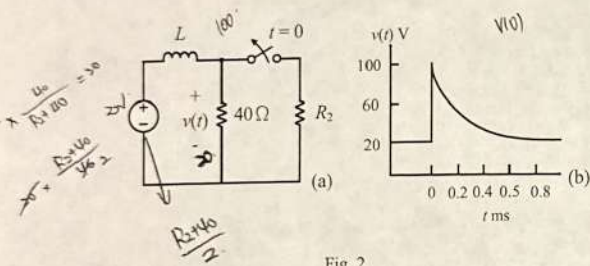2. (11%) Determine the values of L and R_2 considering the circuit shown in Fig. 2(a) and its corresponding plot of voltage across the 40Ω resistor shown in Fig. 2(b).



3. (10%) Find current $i(t)$ of a circuit with sequential switches shown in Fig. 3. While the first switch activates at $t = 1\text{ms}$, the second activates at $t = 2\text{ms}$.

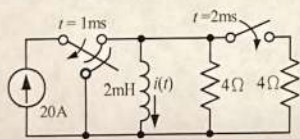


Fig. 3

4. (11%) The circuit in Fig. 4 contains a dependent current controlled current source (CCCS). What restriction shall be added on the gain B to guarantee the stability of the circuit?

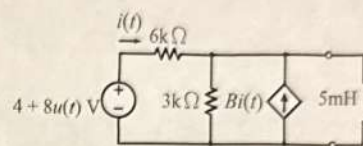


Fig. 4

5. (11%) Determine $v(t)$ for $t > 0$ when the voltage $v_s(t)$ in the circuit shown in Fig. 5 is $v_s(t) = 7 - 14u(t)\text{V}$.

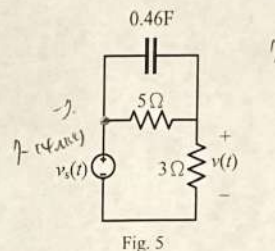


Fig. 5

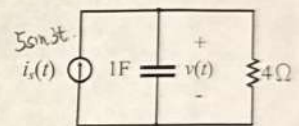


Fig. 6

6. (11%) Find the response $v(t)$ for the circuit shown in Fig. 6. The initial voltage $v(0) = 0$, and the current source is $i_s = 5 \sin 3t$.
7. (10%) For a 1H inductor with $v(0) = 0$ and $i(0) = 0$:
- Determine $v(t)$ when $i(t) = x(t)$, where $x(t)$ is charted in Fig. 7 and $i(t)$ has units of A.
 - Determine $i(t)$ when $v(t) = x(t)$, where $x(t)$ is charted in Fig. 7 and $v(t)$ has units of V.

(There are questions on the back)

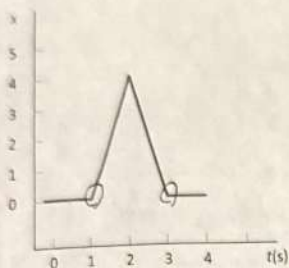


Fig. 7

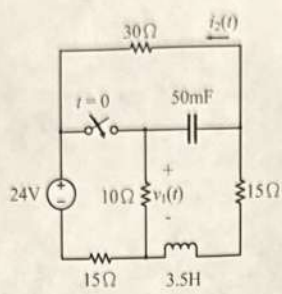


Fig. 8

8. (10%) Determine $v_1(0^-)$, $v_1(0^+)$, $i_2(0^-)$ and $i_2(0^+)$ of the circuit shown in Fig. 8 which is already at steady state when the switch closes at time $t = 0$.
9. (15%) Design a circuit to represent a linear differential equation:

$$\frac{d^2}{dt^2}y(t) + 2\frac{d}{dt}y(t) + 3y(t) = 2x(t)$$

via operation amplifiers along with resistors and capacitors. To simplify the design, assign $C = 1\mu\text{F}$ and $R = 1\text{M}\Omega$ in every elementary integrators, and $R_i = 20\text{k}\Omega$ in every inverting and non-inverting amplifiers.