

8. (10%) Determine the capacitor voltage  $v(t)$  in the circuit of Fig. 7 for  $t > 0$ . Suppose the circuit is steady before the switch closes at  $t = 0$ , and the switch remains closed for 1.5s before reopening.

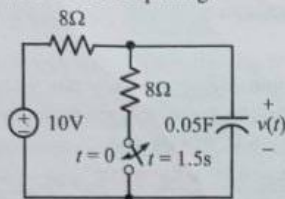


Fig. 7

9. (13%) For an arbitrary 1<sup>st</sup> order differential equation (2), please show and conduct a general solution as (3).

$$\frac{dy(t)}{dt} + ay(t) = f(t)$$

$$\frac{dy(t)}{dt} + ay(t) = f(t) \quad (2)$$

$$y(t) = e^{-at} \int f(t)e^{at} dt + ke^{-at} \quad (3)$$

where  $k$  is a constant.

(2) 式兩邊同乘積分因子  $e^{+at}$ :

$$e^{+at} \frac{dy}{dt} + ay e^{+at} = f(t) e^{+at}$$

$$\frac{d}{dt}(e^{at} y) = f(t) e^{at} \quad \text{--- ①}$$

① 兩邊積分:

$$\int \frac{d}{dt}(e^{at} y) dt = \int f(t) e^{at} dt + C$$

$$e^{at} y = \int f(t) e^{at} dt + C$$

$$y = e^{-at} \int f(t) e^{at} dt + C e^{-at} \quad \text{--- ②}$$

### Midterm Examination

Notice: Please turn off any types of handheld devices, and leave them far from reach. Use only standalone calculators for calculation if it is needed. The examination takes 90 minutes.  
只需繳回答案紙，題目紙請同學保留。

1. (15%) Design a circuit to represent a linear differential equation shown as (1) via operation amplifiers with resistors and capacitors. For simplicity, the elementary integrators use  $C = 1\mu\text{F}$  and  $R = 1\text{M}\Omega$ , and for inverting and non-inverting amplifiers use  $R_i = 20\text{k}\Omega$  as templates to design the circuit.

$$\frac{d^2 y(t)}{dt^2} + 8 \frac{dy(t)}{dt} + 2y(t) = 5f(t) \quad (1)$$

2. (6%) Given  $L_{eq} = 28\text{H}$ , determine the value of the inductance  $L$  in the circuit shown in Fig. 1.

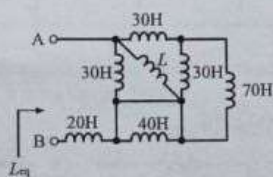


Fig. 1

3. (11%) Determine the inductor current  $i(t)$  in the circuit of Fig. 2 for  $t > 0$  as the circuit has already at steady state before the switch closes at  $t = 0$ .

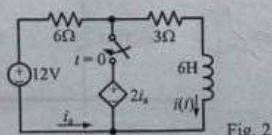


Fig. 2

4. (11%) Derive the inductor current  $i(t)$  for  $t \geq 0$  in the sequential switching circuit shown as Fig. 3.

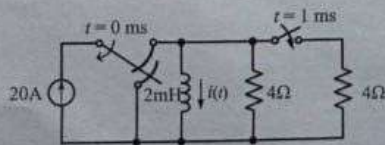


Fig. 3

5. (11%) Determine the output voltage  $v_o(t)$  in the circuit of Fig. 4 as the inductor current  $i_L$  and capacitor voltage  $v_C$  are given by

$$i_L(t) = 0.3(e^{-400t} + e^{-600t})\text{A}, \text{ and } v_C(t) = 15 - 125e^{-400t} + 5e^{-600t}\text{V}, \text{ when } t > 0.$$

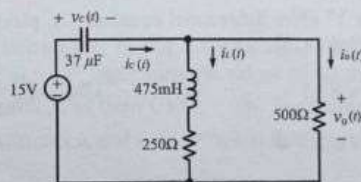


Fig. 4

6. (10%) Determine the voltage  $v_o(t)$  in the circuit of Fig. 5 for  $t > 0$ . Suppose the circuit is in a steady state before the switch opens at time  $t = 0$ .

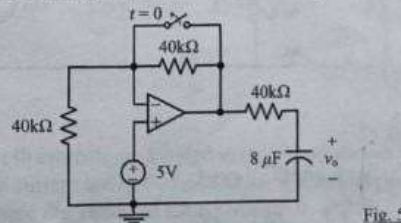


Fig. 5

7. (13%) Determine  $v_o(t)$  for  $t > 0$  in the circuit of Fig. 6.

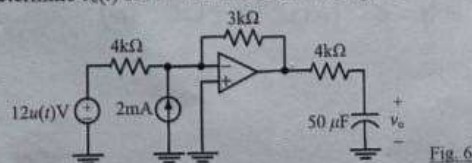


Fig. 6

背面還有題目